



**BITS Pilani**

# Microprocessors & Interfacing


## **IO Interface**

Dr. Gargi Prabhu  
Department of CS & IS
 
# Input Devices

- Input devices are already TTL and compatible, and can be connected to the microprocessor and its interfacing components.
  - or they are switch-based
- Switch-based devices are either open or connected; These are not TTL levels.
  - TTL levels are a logic 0 (0.0 V–0.8 V)
  - or a logic 1 (2.0 V–5.0 V)
- Using switch-based device as TTL-compatible input requires conditioning applied.

- A pull-up resistor ensures when the switch is open, the output signal is a logic 1.
  - when the switch is closed, it connects to ground, producing a valid logic 0 level
- A standard range of values for pull-up resistors is between 1K Ohm and 10K Ohm.





# Input Devices



- Mechanical switch contacts physically bounce when they are closed,
  - which can create a problem if a switch is used as a clocking signal for a digital circuit
    - To prevent problems with bounces, following circuits can be used
- The first version costs more to construct
  - the second costs requires no pull-up resistors and two inverters instead of two NAND gates

# Input Devices

  

Debouncing switch contacts: (a) conventional debouncing and (b) practical debouncing.

# Output Devices




- Output devices are more diverse than input devices, but many are interfaced in a uniform manner.
- Before an output device can be interfaced, we must understand voltages and currents from the microprocessor or TTL interface.
- Voltages are TTL-compatible from the microprocessor of the interfacing element.
  - logic 0 = 0.0 V to 0.4 V
  - logic 1 = 2.4 V to 5.0 V

# Output Devices




- Currents for a processor and many interfacing components are less than for standard TTL.
  - Logic 0 = 0.0 to 2.0 mA
  - logic 1 = 0.0 to 400  $\mu$ A

# Output Devices

 

(a)

 

(b)

- to interface a simple LED to a microprocessor peripheral pin.
  - a transistor driver is used in 11–8(a)
  - a TTL inverter is used in 11–8(b)
- The TTL inverter (standard version) provides up to 16 mA of current at a logic 0 level
  - more than enough to drive a standard LED



# Output Devices



- TTL input signal has minimum value of 2.4 V
- Drop across emitter-base junction is 0.7 V.
- The difference is 1.7 V
  - the voltage drop across the resistor
- The value of the resistor is  $1.7 \text{ V} \div 0.1 \text{ mA}$  or 17K W.
  - as 17K W is not a standard value, an 18K W resistor is chosen

# Output Devices



- TTL input signal has minimum value of 2.4 V
- Drop across emitter-base junction is 0.7 V.
- The difference is 1.7 V
  - the voltage drop across the resistor
- The value of the resistor is  $1.7 \text{ V} \div 0.1 \text{ mA}$  or 17K  $\Omega$ .
  - as 17K  $\Omega$  is not a standard value, an 18K  $\Omega$  resistor is chosen

# How I/O addresses are determined and assigned?



**System Architecture Design:** designed with a specific address space for I/O operations

**Address Decoding:** Address decoding logic maps specific address ranges to particular I/O devices.

**Address Assignment:** the system designer assigns specific I/O addresses to each peripheral device connected to the system. These assignments are typically documented in the system's hardware specifications or datasheets.

**Configuration and Initialization:** During system configuration and initialization, the microprocessor or system firmware may initialize the address decoding logic and configure the I/O addresses for each device.

# How I/O addresses are determined and assigned?



**Programming:** In software development, programmers write device drivers or application software that interacts with the peripheral devices using the assigned I/O addresses. These software components use the addresses defined in the system hardware to access and control the devices.

**Testing and Verification:** Before deployment, the system undergoes testing and verification to ensure that the assigned I/O addresses function correctly and that the peripheral devices respond as expected to I/O operations.

# I/O Port Address Decoding

---

- Very similar to memory address decoding, especially for memory-mapped I/O devices.
- The difference between memory decoding and isolated I/O decoding is the number of address pins connected to the decoder.
- In the personal computer system, we always decode all 16 bits of the I/O port address.


# I/O Port Address Decoding

- Fixed I/O instruction uses an 8-bit I/O port address that on  $A_{15}-A_0$  as 0000H–00FFH.
  - we often decode only address connections  $A_7-A_0$  for an 8-bit I/O port address
- The DX register can also address I/O ports 00H–FFH.
- If the address is decoded as an 8-bit address, we can never include I/O devices using a 16-bit address.
  - the PC never uses or decodes an 8-bit address

# I/O Port Address Decoding

- Fixed I/O instruction uses an 8-bit I/O port address that on  $A_{15}-A_0$  as 0000H–00FFH.
  - we often decode only address connections  $A_7-A_0$  for an 8-bit I/O port address
- The DX register can also address I/O ports 00H–FFH.
- If the address is decoded as an 8-bit address, we can never include I/O devices using a 16-bit address.
  - the PC never uses or decodes an 8-bit address


# I/O Port Address Decoding

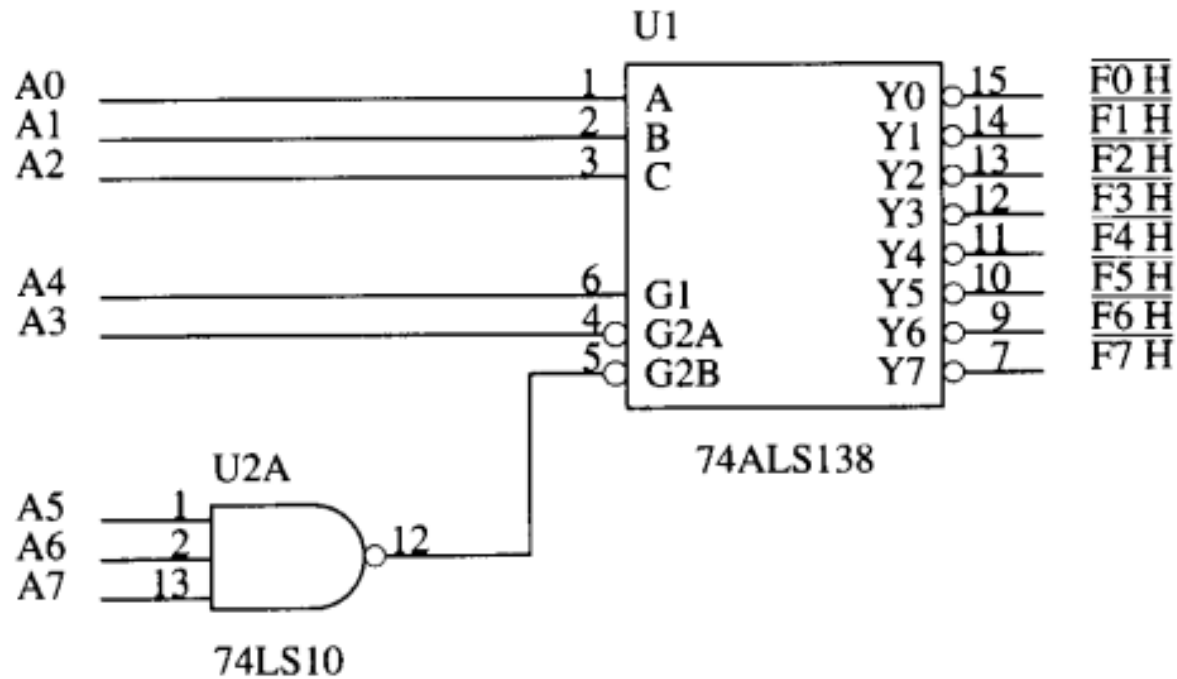

A port decoder that decodes 8-bit I/O ports. This decoder generates active low outputs for ports F0H–F7H



# I/O Port Address Decoding

 

A port decoder that decodes 8-bit I/O ports. This decoder generates active low outputs for ports F0H-F7H.

# VHDL code for the decoder for PLD



```
library ieee;
use ieee.std_logic_1164.all;

entity DECODER_11_11 is
port (
    A7, A6, A5, A4, A3, A2, A1, A0: in STD_LOGIC;
    D0, D1, D2, D3, D4, D5, D6, D7: out STD_LOGIC
);

end;

architecture V1 of DECODER_11_11 is
begin
    D0 <= not( A7 and A6 and A5 and A4 and not A3 and not A2 and not A1 and
               not A0 );
    D1 <= not( A7 and A6 and A5 and A4 and not A3 and not A2 and not A1 and
               A0 );
    D2 <= not( A7 and A6 and A5 and A4 and not A3 and not A2 and A1 and
               not A0 );
```

# VHDL code for the decoder for PLD



```
D3 <= not( A7 and A6 and A5 and A4 and not A3 and not A2 and A1 and
          A0 );
D4 <= not( A7 and A6 and A5 and A4 and not A3 and A2 and not A1 and
          not A0 );
D5 <= not( A7 and A6 and A5 and A4 and not A3 and A2 and not A1 and
          A0 );
D6 <= not( A7 and A6 and A5 and A4 and not A3 and A2 and A1 and
          not A0 );
D0 <= not( A7 and A6 and A5 and A4 and not A3 and A2 and A1 and
          A0 );


end V1;
```

# Decoding 16-bit I/O Port Addresses



- PC systems typically use 16-bit I/O addresses.
  - 16-bit addresses rare in embedded systems
- The difference between decoding an 8-bit and a 16-bit I/O address is that eight additional address lines ( $A_{15}$ – $A_8$ ) must be decoded.

# Decoding 16-bit I/O Port Addresses

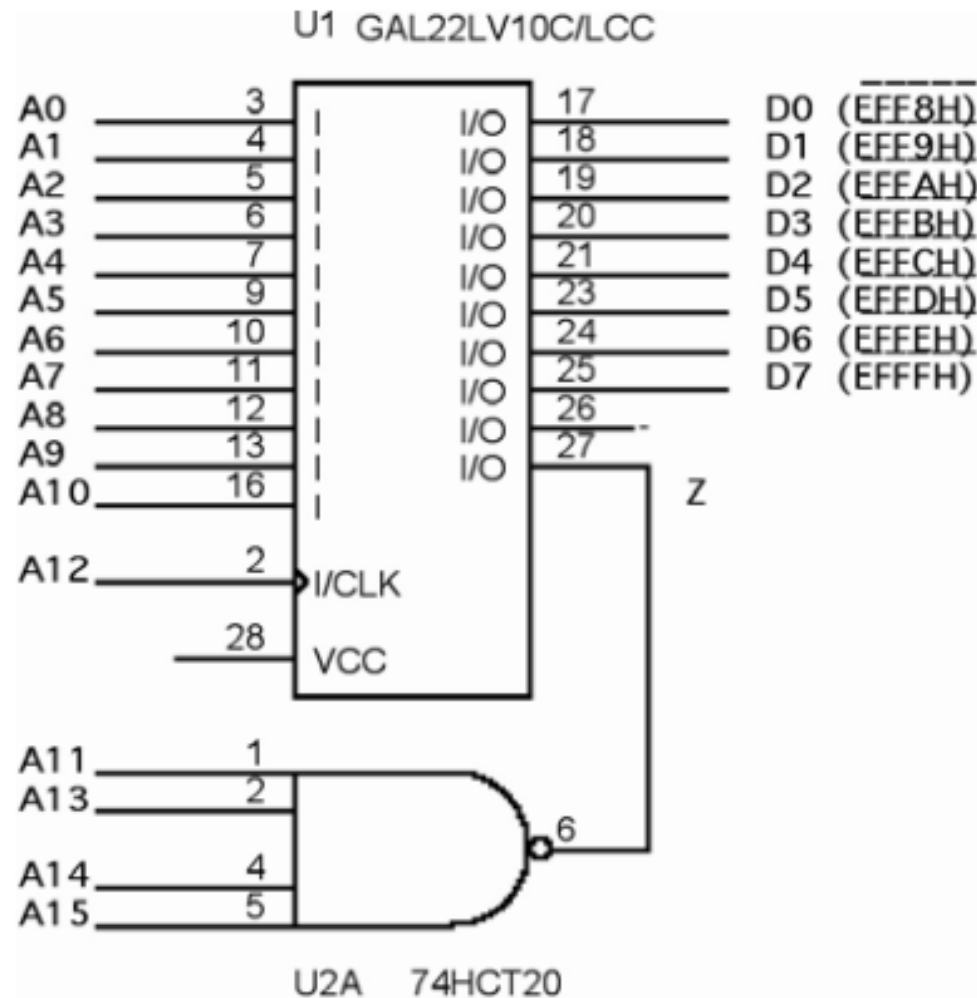

# VHDL Code

innovate

achieve

lead

```
entity DECODER_11_12 is
port (
    Z, A12, A10, A9, A8, A7, A6, A5, A4, A3, A2, A1, A0: in STD_LOGIC;
    D0, D1, D2, D3, D4, D5, D6, D7: out STD_LOGIC
);
end;

architecture V1 of DECODER_11_12 is
begin
    D0 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and not A2 and not A1 and not A0 );
    D1 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and not A2 and not A1 and A0 );
    D2 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and not A2 and A1 and not A0 );
    D3 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and not A2 and A1 and A0 );
    D4 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and A2 and not A1 and not A0 );
    D5 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and A2 and not A1 and A0 );
    D6 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and A2 and A1 and not A0 );
    D7 <= not ( not Z and not A12 and A10 and A9 and A8 and A7 and A6 and A5
               and A4 and A3 and A2 and A1 and A0 );


end V1;
```

# 8- and 16-Bit Wide I/O Ports



- Data transferred to an 8-bit I/O device exist in one of the I/O banks in a 16-bit processor such as 80386SX.
- The I/O system on such a microprocessor contains two 8-bit memory banks.
- Fig 11–13 shows separate I/O banks for a 16-bit system such as 80386SX.
- Because two I/O banks exist, any 8-bit I/O write requires a separate write.
 
# The I/O banks found in the 8086, 80186, 80286, and 80386SX






# 8- and 16-Bit Wide I/O Ports



- I/O reads don't require separate strobes
  - as with memory, the processor reads only the byte it expects and ignores the other byte
  - a read can cause problems when an I/O device responds incorrectly to a read operation

innovate      achieve      lead

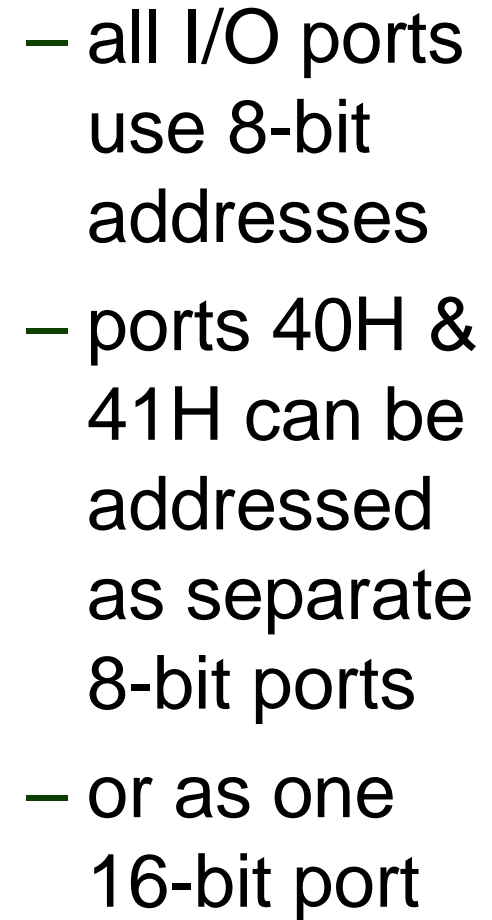

# VHDL Code



```
-- VHDL code for the decoder of Figure 11-14

library ieee;

use ieee.std_logic_1164.all;
entity DECODER_11_14 is

port (
    BHE, IOWC, A7, A6, A5, A4, A3, A2, A1, A0: in STD_LOGIC;
    D0, D1: out STD_LOGIC
);

end;

architecture V1 of DECODER_11_14 is

begin

    D0 <= BHE or IOWC or A7 or not A6 or A5 or A4 or A3 or A2 or A1 or A0;
    D1 <= BHE or IOWC or A7 or not A6 or A5 or A4 or A3 or A2 or A1 or
        not A0;


end V1;
```

# 16-bit Port



- The PLD decoder does not have a connection for address bits BLE ( $A_0$ ) and BHE because the signals don't apply to 16-bit-wide devices.
- The program for the PLD shows how the enable signals are generated for the three-state buffers (74HCT244) used as input devices.

# 16-bit Port

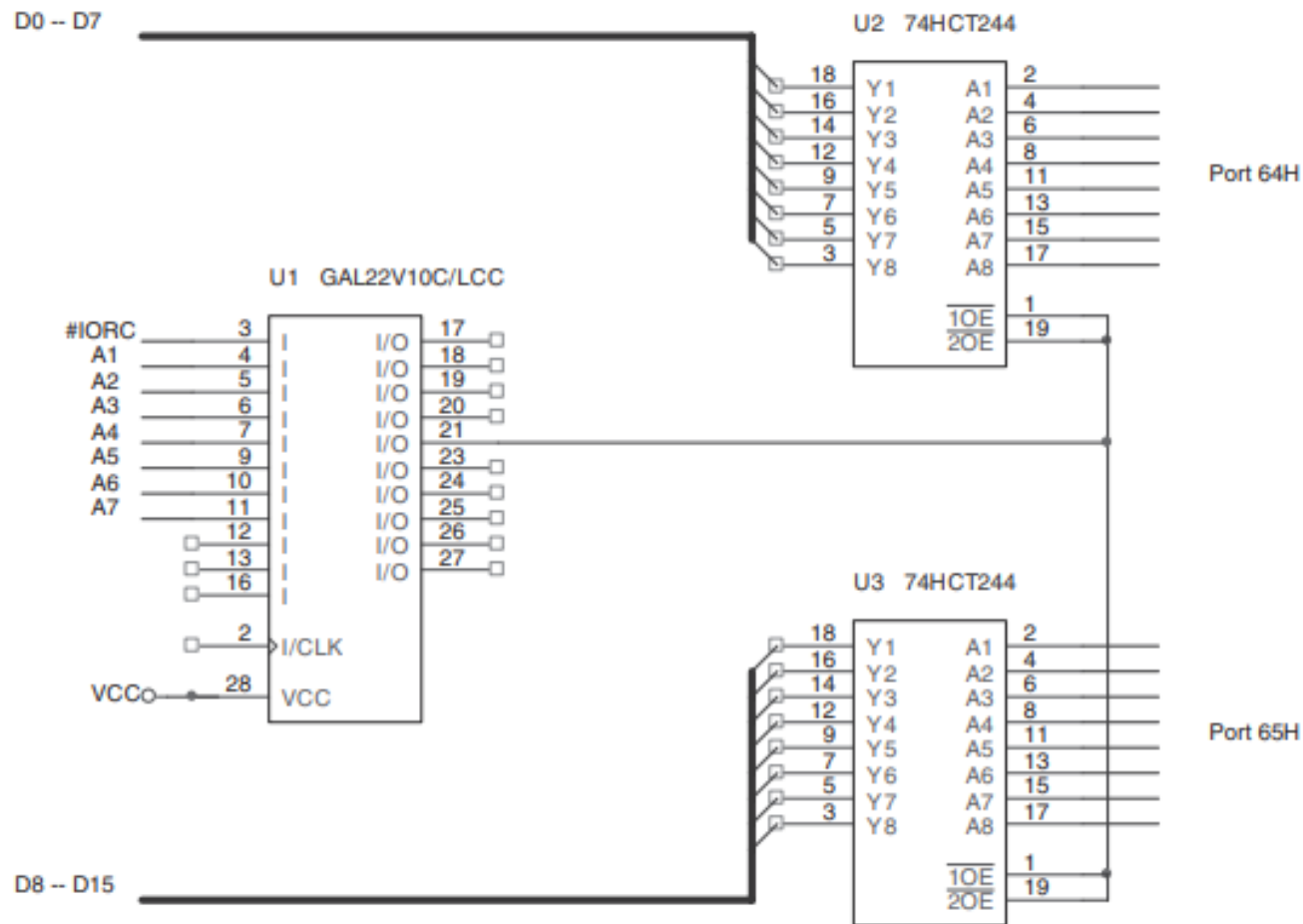

# VHDL Code



```
-- VHDL code for the decoder of Figure 11-15

library ieee;
use ieee.std_logic_1164.all;

entity DECODER_11_15 is

port (
    IORC, A7, A6, A5, A4, A3, A2, A1: in STD_LOGIC;
    D0: out STD_LOGIC
);

end;

architecture V1 of DECODER_11_15 is

begin

    D0 <= IORC or A7 or not A6 or not A5 or A4 or A3 or not A2 or A1;

end V1;
```



**BITS Pilani**  
Pilani Campus



# Thank You