



**BITS Pilani**

# Microprocessors & Interfacing

# **Memory Interface**

Dr. Gargi Prabhu  
Department of CS & IS

# Common types of memory

---


- Read-only memory (ROM)
- Flash memory (EEPROM)
- Static random access memory (SRAM)
- Dynamic random access memory (DRAM)
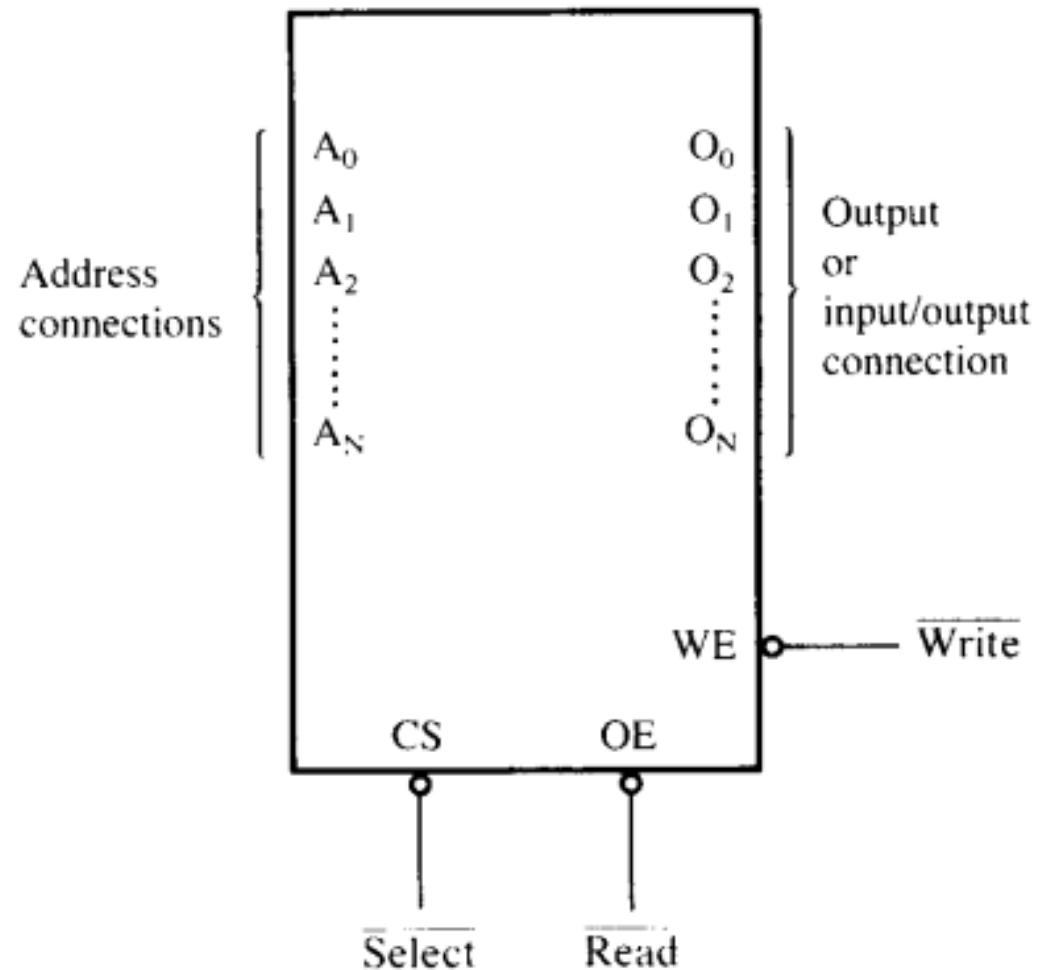
# Memory Device



Pin connections common to all memory devices are:

- Address inputs
- Data outputs or input/outputs
- Some type of selection input
- At least one control input used to select a read or write operation



# Address Connections



- A 1K memory device has 10 address pins (A0–A9)
- 10 address inputs are required to select any of its 1024 memory locations
- It takes a 10-bit binary number (1024 different combinations) to select any single location on a 1024-location device

# Data Connections

---

- All memory devices have a set of data outputs or input/outputs.
- The data connections are the points at which data are entered for storage or extracted for reading.
- Data pins on memory devices are labeled D0 through D7 for an 8-bit-wide memory
- An 8-bit-wide memory device is often called a byte-wide memory

# Selection Connections

- Each memory device has an input—sometimes more than one—that selects or enables the memory device.
- This type of input is most often called a chip select ( $CS'$ ), chip enable ( $CE'$ ), or simply select ( $S'$ ) input.
- RAM memory generally has at least one  $CS'$  or  $S'$  input, and ROM has at least one  $CE'$ .
- If the  $CS', S', CE'$  or input is active (a logic 0), the memory device performs a read or write operation; if it is inactive (a logic 1), the memory device cannot do a read or a write because it is turned off or disabled.
- If more than one connection is present, all must be activated to read or write data

# Control Connections



- All memory devices have some form of control input or inputs.
- A ROM usually has only one control input, while a RAM often has one or two control inputs.

ROM - output enable ( $OE'$ ) or gate ( $G'$ )

-  $OE'$  and  $CE'$  are both active, output is enabled

RAM –  $R/W'$  along with  $CS'$  – can read and write

-  $WE'$  and  $OE'$  ( or  $G'$ ) – can read and write

# ROM



- Read-only memory (ROM) permanently stores programs and data that are resident to the system and must not change when power supply is disconnected.
- Known as nonvolatile memory
- ROM is often used to store firmware, BIOS, and other critical system software that needs to be permanently stored and not modified during normal operation



# EPROM




- EPROM (erasable programmable read-only memory), a type of ROM, is more commonly used when software must be changed often
- EPROM is erasable if exposed to high-intensity ultraviolet light for about 20 minutes or so, depending on the type of EPROM
- EPROMs are used in applications where occasional updates or changes to the stored data are necessary but not frequent enough to warrant the use of EEPROM or flash memory.

# 2716, 2K\*8 EPROM



PIN CONFIGURATION

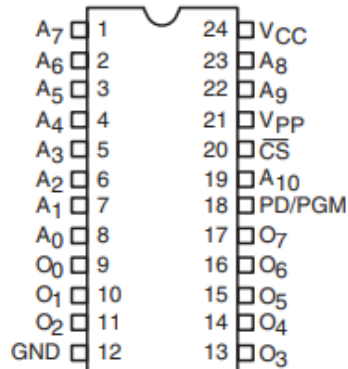


PIN NAMES

A <sub>0</sub> –A <sub>10</sub>	ADDRESSES
PD/PGM	POWER DOWN/PROGRAM
$\overline{\text{CS}}$	CHIP SELECT
O <sub>0</sub> –O <sub>7</sub>	OUTPUTS

MODE SELECTION

MODE \ PINS	PD/PGM (18)	$\overline{\text{CS}}$ (20)	V <sub>PP</sub> (21)	V <sub>CC</sub> (24)	OUTPUTS (9-11, 13-17)
Read	V <sub>IL</sub>	V <sub>IL</sub>	+5	+5	DOUT
Deselect	Don't care	V <sub>IH</sub>	+5	+5	High Z
Power Down	V <sub>IH</sub>	Don't care	+5	+5	High Z
Program	Pulsed V <sub>IL</sub> to V <sub>IH</sub>	V <sub>IH</sub>	+25	+5	DIN
Program Verify	V <sub>IL</sub>	V <sub>IL</sub>	+25	+5	DOUT
Program Inhibit	V <sub>IL</sub>	V <sub>IH</sub>	+25	+5	High Z

BLOCK DIAGRAM

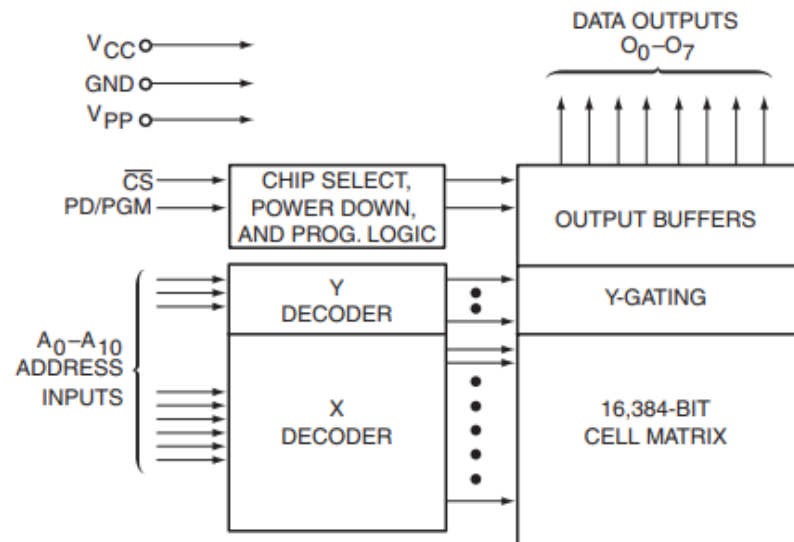


# How chip is connected


innovate

achieve

lead

 

# The timing diagram of 2716 EPROM

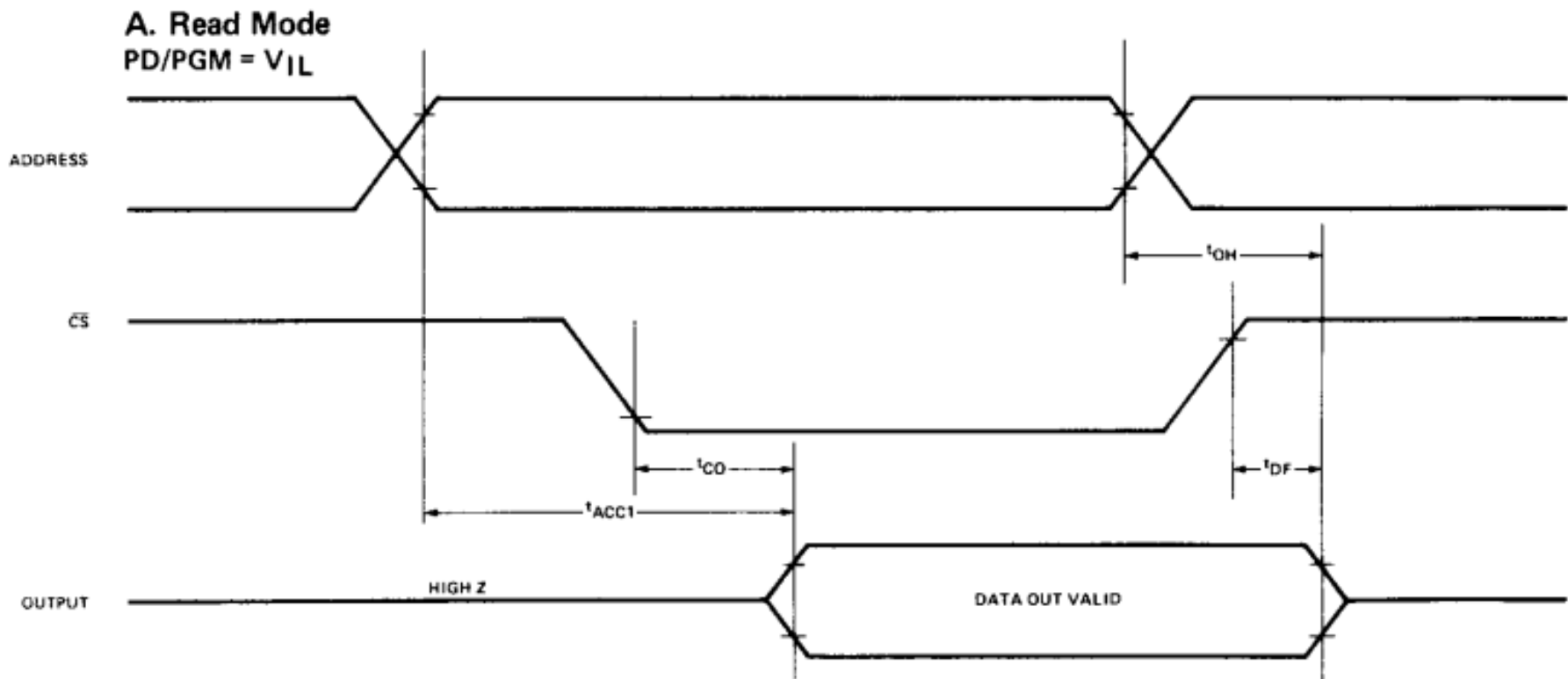

# Memory Access Time

---


- $T_{ACC}$  is measured from the appearance of the address at the address inputs until the appearance of the address at the address output
- Basic speed of EPROM is 450 ns
- Wait states are required to ensure smooth operations.

# Static RAM



- Static RAM memory devices retain data for as long as DC power is applied.
- Because no special action (except power) is required to retain stored data, these devices are called static memory.
- Also called volatile memory because they will not retain data without power.

TMS4016 . . . NL PACKAGE  
(TOP VIEW)

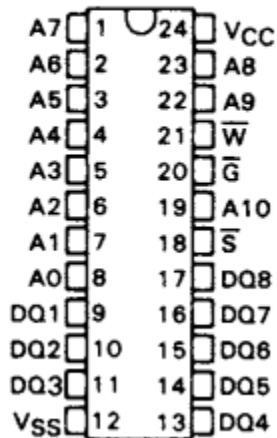

PIN NOMENCLATURE	
A0 – A10	Addresses
DQ1 – DQ8	Data In/Data Out
$\overline{G}$	Output Enable
$\overline{S}$	Chip Select
VCC	+ 5-V Supply
VSS	Ground
$\overline{W}$	Write Enable

# Dynamic RAM (DRAM) Memory




- DRAM is essentially the same as SRAM, except that it retains data for only 2 or 4 ms on an integrated capacitor
- In DRAM, the entire contents of the memory are refreshed with 256 reads in a 2- or 4-ms interval
- Refreshing also occurs during a write, a read, or during a special refresh cycle
- DRAM is widely used as the main memory in computers and other digital devices due to its cost-effectiveness and high storage capacity.
- Another disadvantage of DRAM memory is that it requires so many address pins that the manufacturers have decided to multiplex the address inputs.

# TMS4464, 64K × 4 dynamic RAM


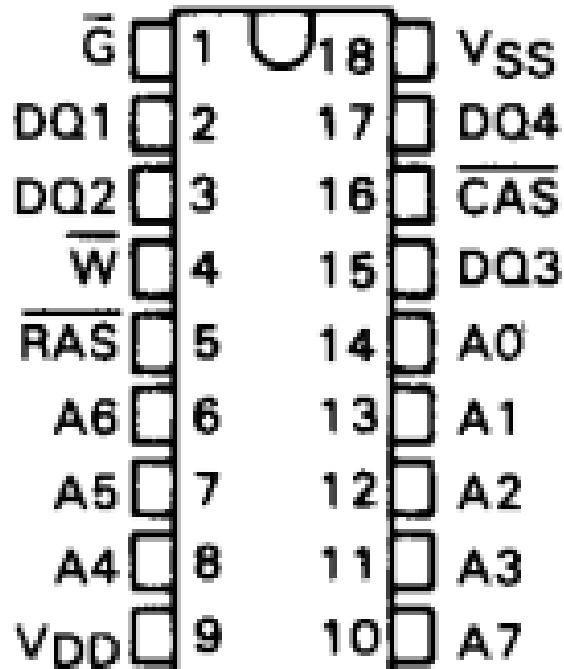
## TMS4464 . . . JL OR NL PACKAGE (TOP VIEW)




(a)

PIN NOMENCLATURE	
A0-A7	Address Inputs
$\overline{CAS}$	Column Address Strobe
DQ1-DQ4	Data-In/Data-Out
$\overline{G}$	Output Enable
$\overline{RAS}$	Row Address Strobe
VDD	+5-V Supply
VSS	Ground
$\overline{W}$	Write Enable


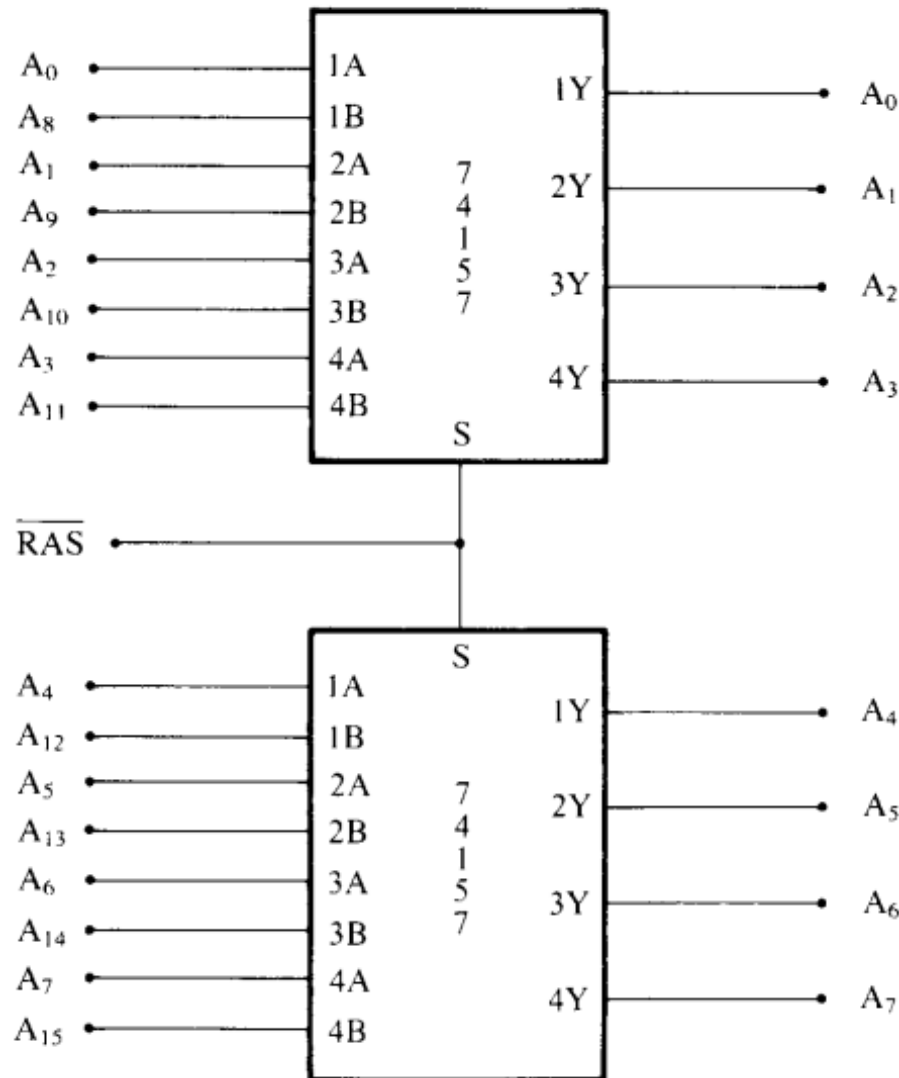
# Address multiplexer for the TMS4464 DRAM



# References



- <https://www.youtube.com/watch?v=P0oJPvwca6I>



**BITS Pilani**  
Pilani Campus



# Thank You