




BITS Pilani


Microprocessors & Interfacing **Hardware Design**

Dr. Gargi Prabhu
Department of CS & IS

Interfacing 8284 with 8086

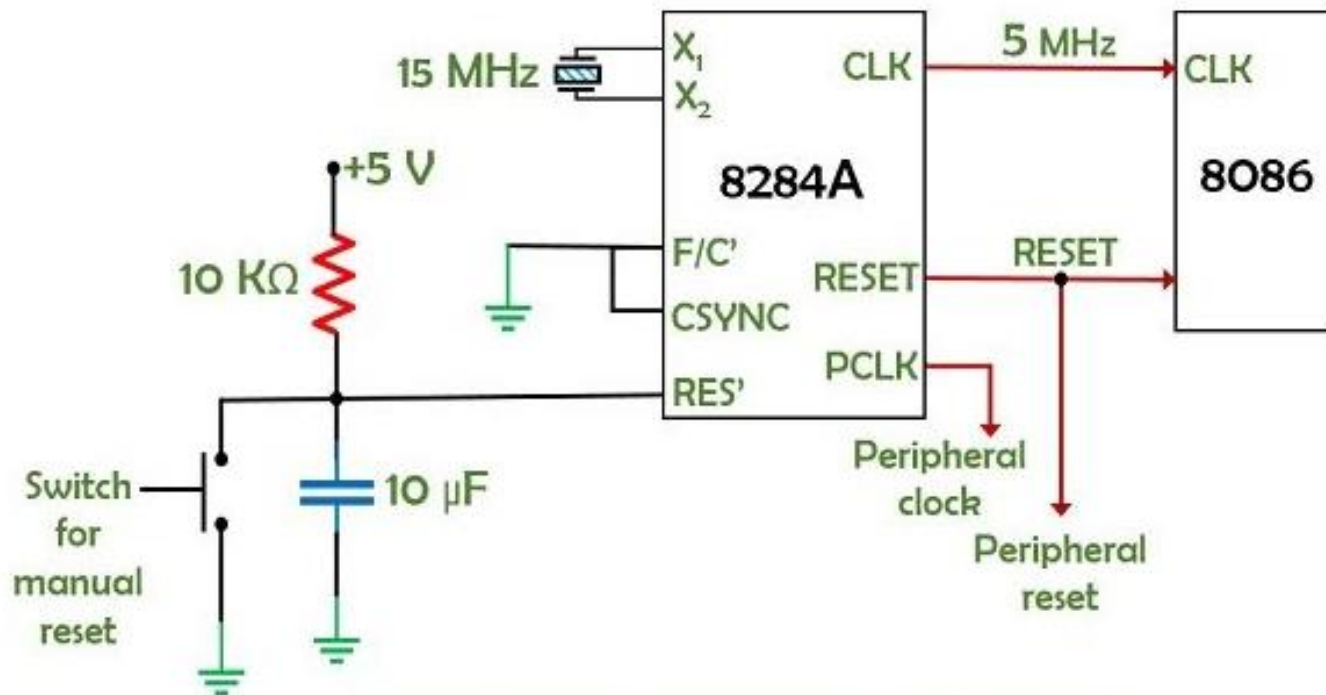

Min Max Mode

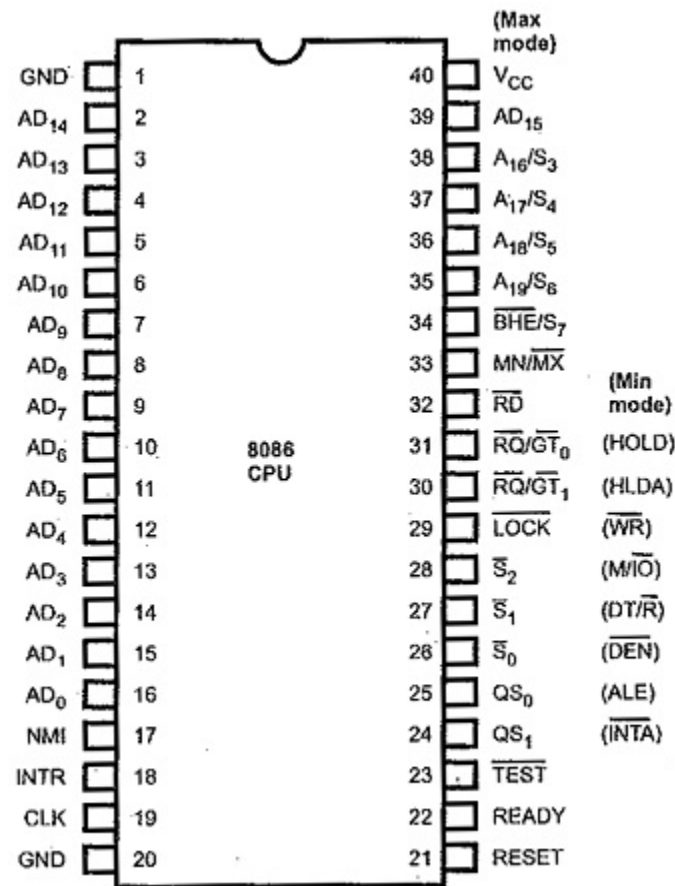

Difference between Minimum & Maximum Mode





Minimum mode	Maximum mode
There can be only one processor.	There can be multiple processors.
Performance is slower.	Performance is faster.
The circuit is simple.	The circuit is complex.
Multiprocessing cannot be performed.	Multiprocessing can be performed.
MN/MX is 1 to indicate the minimum mode.	MN/MX is 0 to indicate the maximum mode
The 8086 generates INTA for interrupt acknowledgment.	The 8288 Bus Controller generates the interrupt acknowledgment signal (INTA).
The 8086 itself provides an ALE for the latch.	Because there are several processors, the 8288 bus controller provides ALE for the latch.
The system is more affordable.	The system costs more money.
It is used for small systems.	It is used for large systems.
The multiprocessor setup is not supported.	The multiprocessor configuration is accepted.

Demultiplexing the Buses

All computer systems have three buses:

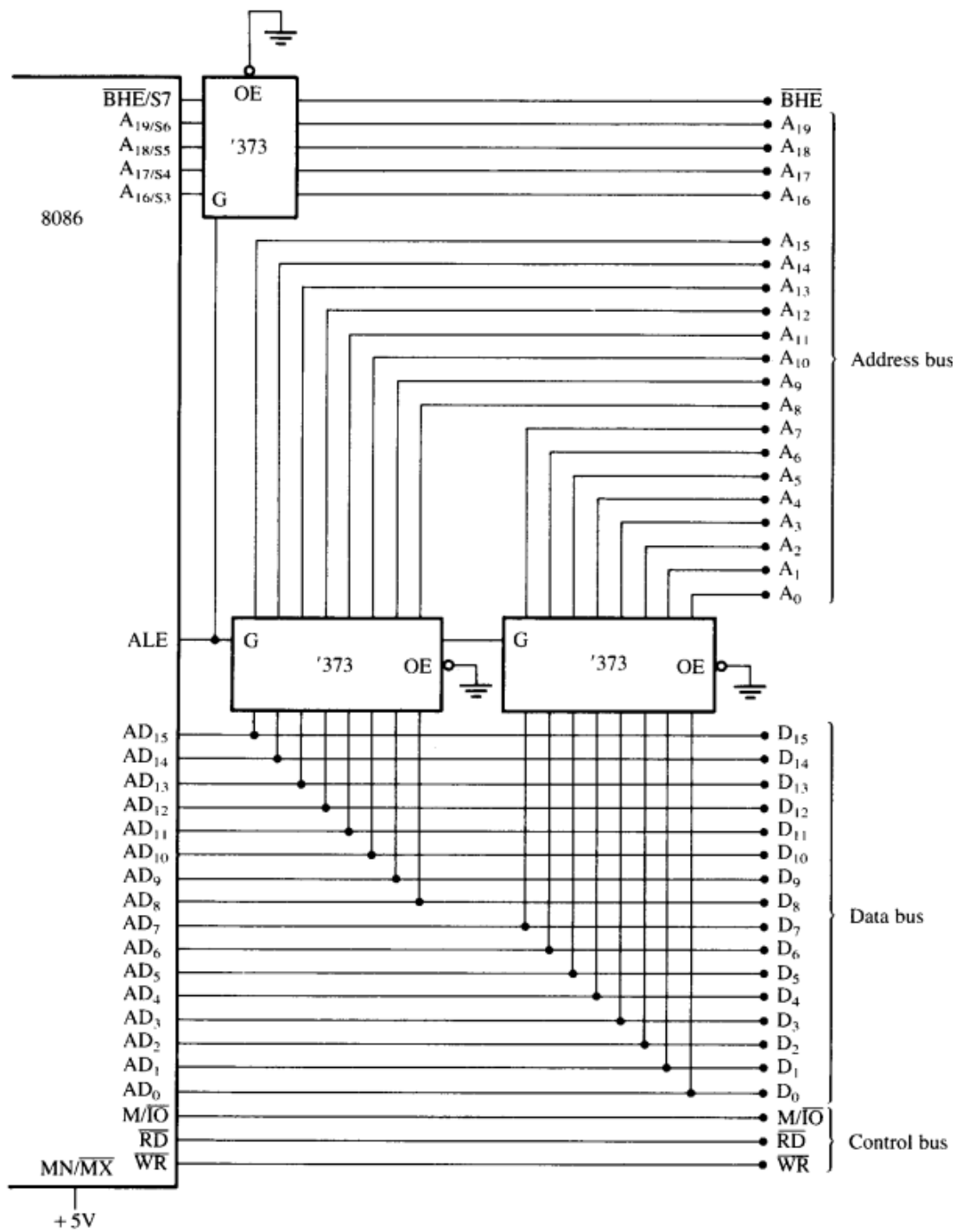- (1) an address bus that provides the memory and I/O with the memory address or the I/O port number
 - (2) a data bus that transfers data between the micro processor and the memory and I/O in the system
 - (3) a control bus that provides control signals to the memory and I/O.
- Two 74LS373 or 74LS573 transparent latches are used to demultiplex the address/data luses



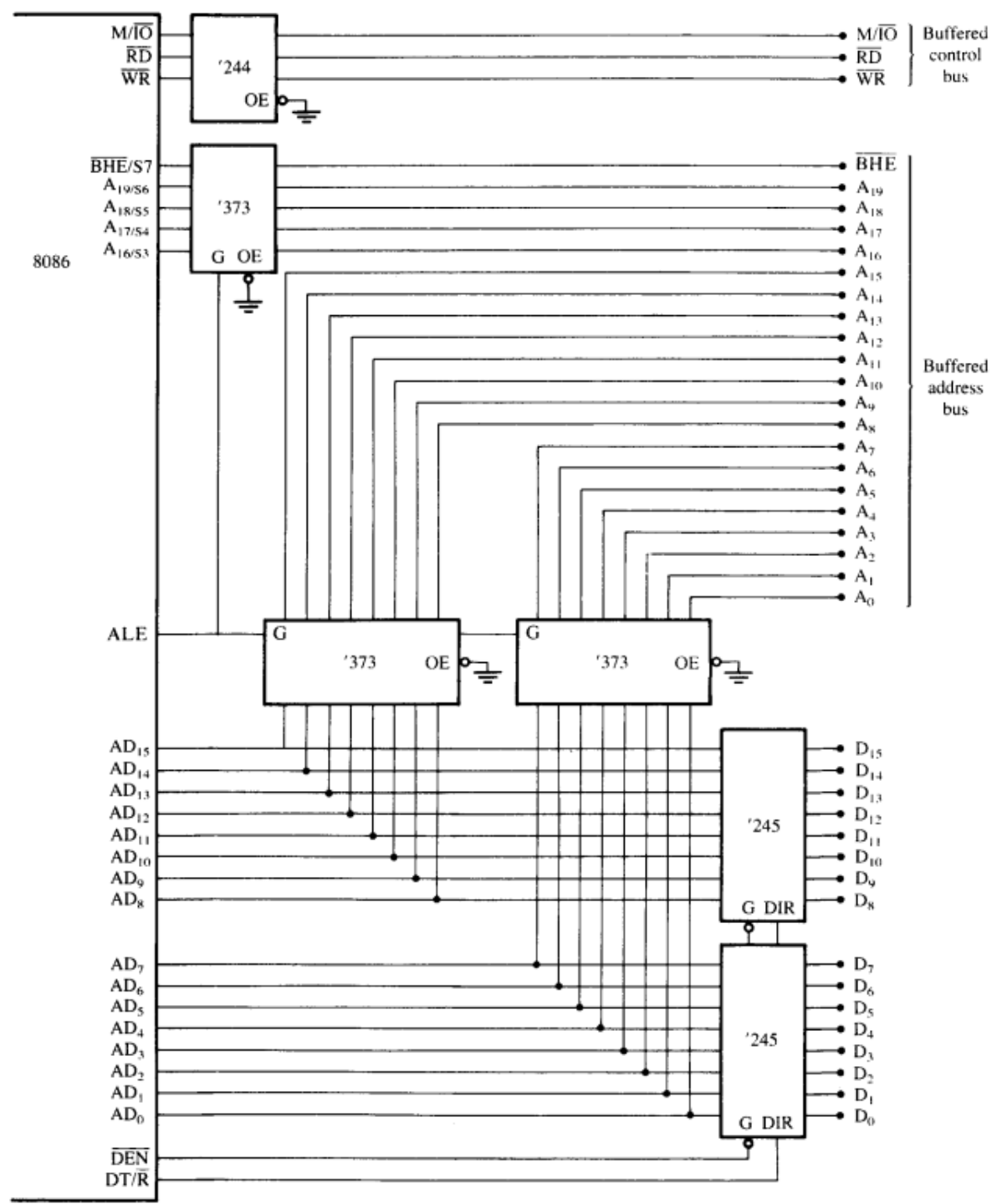

Bus Timing



- The 8086/8088 microprocessors use the memory and I/O in periods called bus cycles.
- Each bus cycle equals four system-clocking periods (T states)
- If the clock is operated at 5 MHz , one 8086 bus cycle is complete inns
- This means that the microprocessor reads or writes data between itself and memory or I/O at a maximum rate of..... million times a second.

Generation of control signal



M/IO'	RD'	WR'	Bus cycle
1	0	1	MEMR'
1	1	0	MEMW'
0	0	1	IOR'
0	1	0	IOW'

Bus Timing



During T1

- The address of the memory or I/O location is sent out via the address bus and the address/data bus connections.
- Control signals are also sent out

During T2,

- The 8086/8088 microprocessors issue the RD' or WR' signal, DEN' , and in the case of a write, the data to be written appear on the data bus.
- The DEN' signal turns on the data bus buffers, if they are present in the system, so the memory or I/O can receive data to be written, or so the microprocessor can accept the data read from the memory or I/O for a read operation

Bus Timing




During T3

- If the bus cycle happens to be a read bus cycle, the data bus is sampled at the end of T3


During T4

- All bus signals are deactivated in preparation for the next bus cycle.
- 8086/8088 samples the data bus connections for data that are read from memory or I/O.
- At the trailing edge of the \overline{WR} signal transfers data to the memory or I/O, which activates and writes when the \overline{WR} signal returns to a logic 1 level

Bus Timing

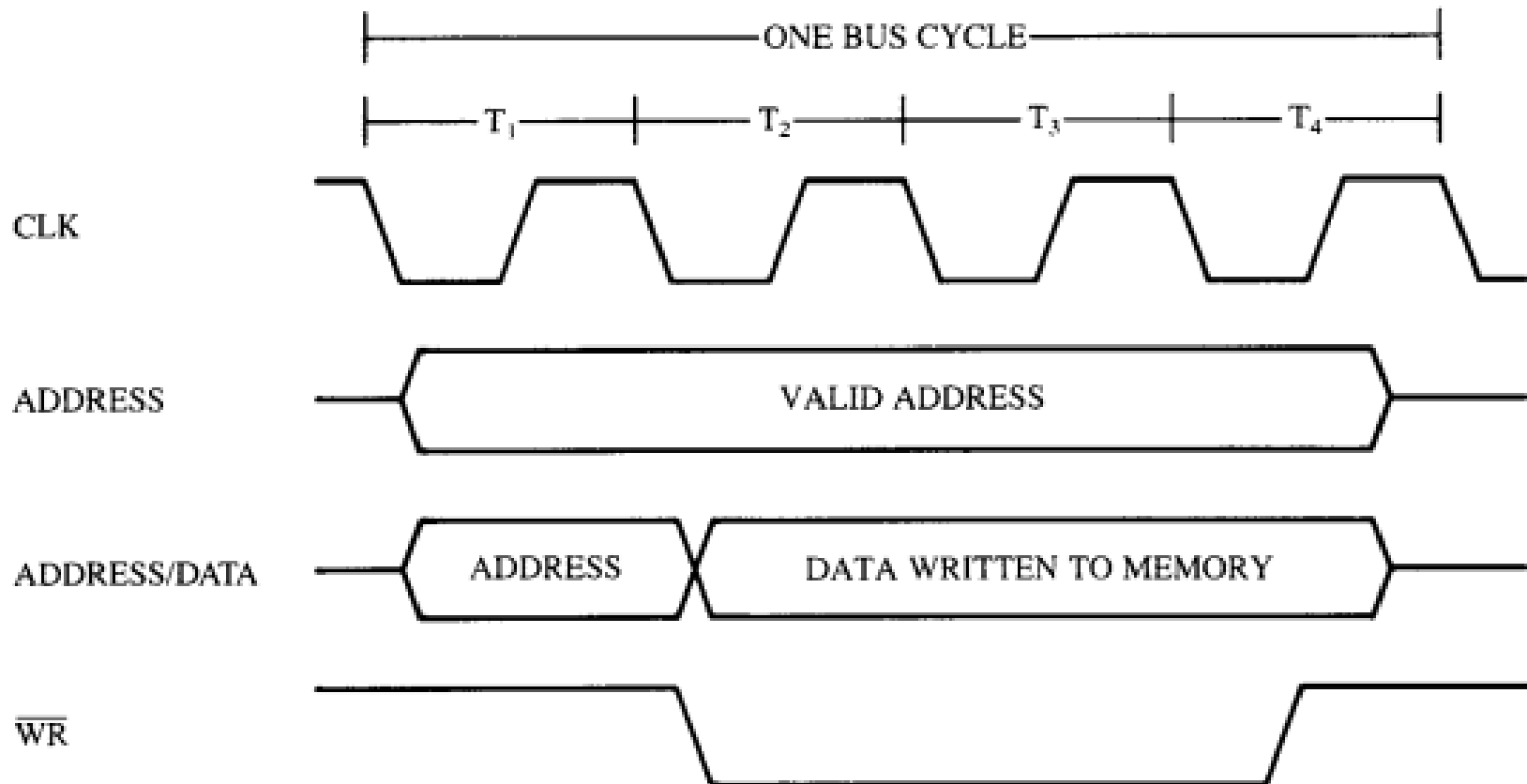

Read Timing

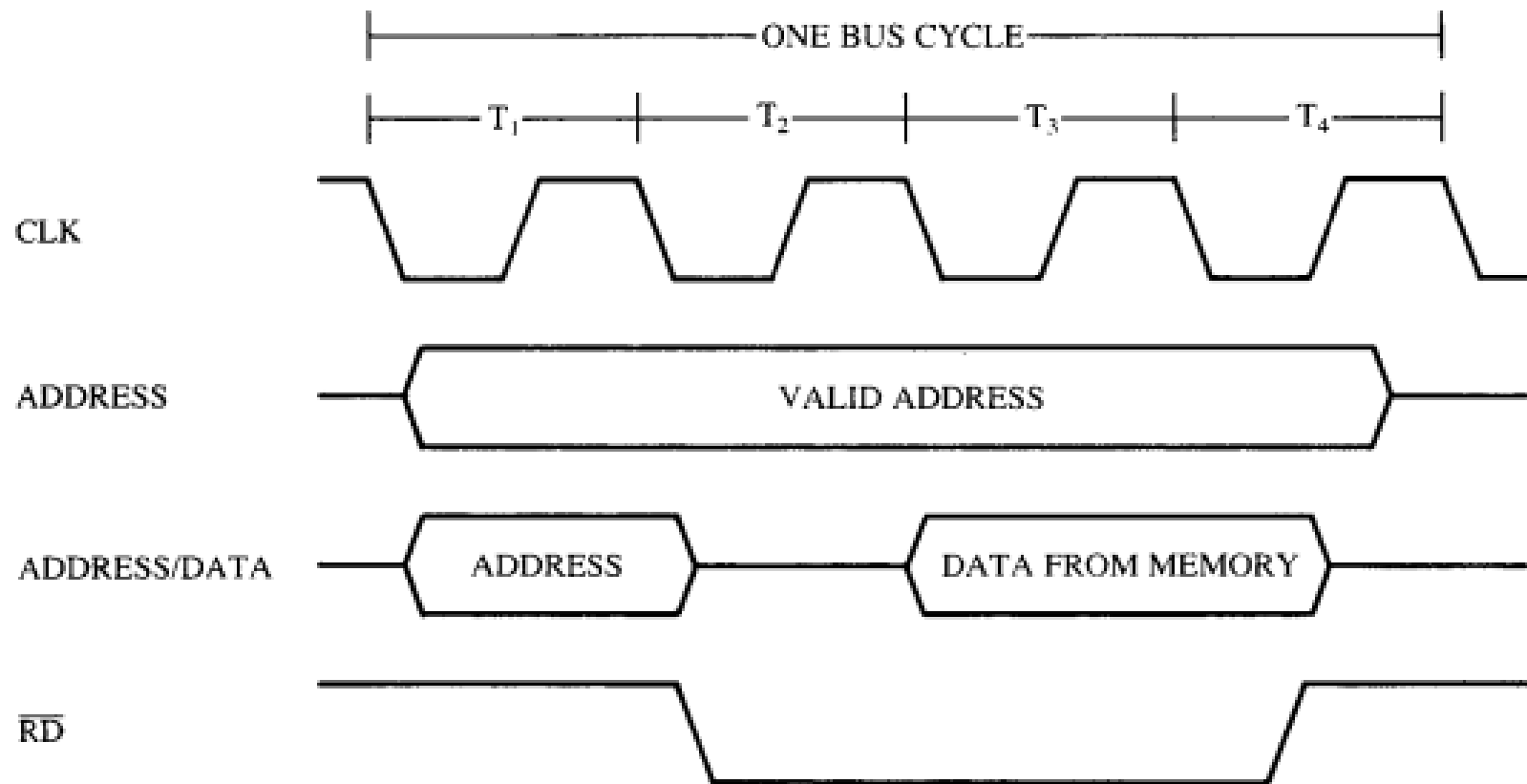



BITS Pilani
Pilani Campus



Thank You